

**University of Bahrain**  
**College of Information Technology**  
*Department of Computer Engineering*

**ITCE 202: Digital Logic  
Test 1**

**Time: 1:00 hour**

**Date: November 2<sup>nd</sup>, 2004**

Question	Marks	Score
1	24	
2	18	
3	18	
4	20	
5	20	
Total	100	

ID. No.	Name:	Sec.:
---------	-------	-------

---

**Show all your work.**

---

**Q1 ( 24 points)**  
**(4 points) (a) Convert  $(326.5)_8$  to Hexadecimal**

**(4 points) (b) The following number 1 1 1 0 0 0 0 1 1 0 0 1 0 1 1 1 represents decimal digits in 4-3-2-1 weighted code. Find its equivalent in BCD weighted code.**



**(8 Points) (c) Divide in binary 1 1 1 0 1 00 by 1 0 1 0 and approximate the result up to two fraction bits.**

**(8 Points) (d) Perform the binary addition of the two decimal numbers (+39) and (-28), assume that the numbers are represented in 2's complement form.**

**Q2- ( 18 points)**

**(10 Points) (a) Simplify the following function to a minimum Sum of product form**

$$Z = A \bar{B} C + F + (A \bar{B} D + C \bar{D})(\bar{C} E + \bar{F} + A \bar{B} D)$$




**(8 Points)** (b) Given that:  $Z = \overline{E}G (A \oplus B + \overline{C}E)(\overline{A} + BG)$

Use De'Morgan's Theorem to find  $\overline{Z}$ . Express your answer in a sum of product form (Do not simplify).


**Q3 (18 points)**

For the circuit shown in figure 1, find:

 

**(10 Points)** (a)  $Z$  in a standard Sum of product (minterm form)

 **(8 Points)** (b)  $\overline{Z}$  in a standard product of sums (algebraic form).



**Q4 ( 20 points)**

Realised the function Z given by the following equation using the minimum number of 2-inputs NAND gates only.

$$Z = \overline{A} B C \overline{D} + E \overline{F} + B \overline{D} \overline{G} + B \overline{D} \overline{E}$$

**Q5- ( 20 points)**

Given the Boolean function:  $F = \overline{A}CD + A\overline{B}\overline{C}\overline{D} + ABC + A\overline{C}D + \overline{A}\overline{B}\overline{C}D$

Assuming that the inputs ABCD = 0000, ABCD = 1000, and ABCD = 1101 never occur, find a minimum NOR-NOR network implementation for F.



**University of Bahrain**  
**College of Information Technology**  
*Department of Computer Engineering*

**ITCE 202: Digital Logic**  
**Test II**

**Time: 1:00 hour**

**Date: December 14, 2004**

Question	Marks	Score
1	20	
2	20	
3	20	
4	20	
5	20	
<b>Total</b>	<b>100</b>	

**Q1 (20 points)**

A combinational Logic Circuit accepts two 4-bit binary numbers  $A = A_3 A_2 A_1 A_0$ , and  $B = B_3 B_2 B_1 B_0$  and generates a single output Z such that:

$$Z = 1 \quad \text{if} \quad A + B + 7 \geq 12 \quad \text{else} \quad Z = 0$$


Use any necessary ICs and logic gates to implement the combinational circuit.

**Q2(20 points)**

Use 3-to-8 decoder(s) with enable to implement a code converter combinational circuit that takes as its inputs an Excess-3 code digit and outputs its equivalent BCD digit.


 
**Q3 (20 points)**

Express F in a S-O-P form (Do not simplify)



  **Q4(20 points)**

Complete the following timing diagram for the circuit shown below.



**Q5(20 points)**

A gated Latch has two inputs G, and L behaves as follows: If  $G = 0$  the latch does not change its state. If  $G=1$ , the next state of the latch is equal to its input L

(a) Derive the characteristic equation of the G-L latch.

(b) Show how a J-K latch can be converted to a G-L latch.

